

## Low Cost, High Voltage, Programmable Gain In-Amp Using the **AD5292** Digital Potentiometer and the **AD8221** In-Amp

### CIRCUIT FUNCTION AND BENEFITS

The circuit shown in Figure 1 provides a low cost, high voltage, programmable gain instrumentation amplifier (in-amp) using the **AD5292** digital potentiometer and the **AD8221** in-amp.

The circuit offers 1024 different gain settings that are controllable through a digital serial peripheral interface (SPI). The  $\pm 1\%$  resistor tolerance performance of the **AD5292** provides low gain error over the full resistor range, as shown in Figure 2.

The circuit provides a high performance in-amp that delivers a high common-mode rejection ratio (CMRR) over frequency and dynamic programmable gain for both single-supply operation at +30 V and dual-supply operation at  $\pm 15$  V. In addition, the **AD5292** has an internal 20 $\times$  programmable memory that allows the user to customize the in-amp gain at power-up.

The circuit provides accurate, low noise, high gain and is well suited for signal instrumentation conditioning, precision data acquisition, biomedical analysis, and aerospace instrumentation.

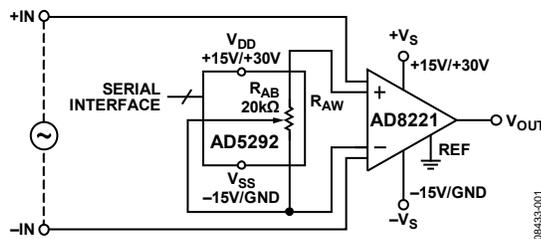


Figure 1. Programmable Gain In-Amp (Simplified Schematic, All Connections Not Shown)

**TABLE OF CONTENTS**

Circuit Function and Benefits..... 1  
Revision History ..... 2  
Circuit Description..... 3  
Common Variations..... 4  
Reference..... 4

**REVISION HISTORY**

**8/2018—Rev. A to Rev. B**

Document Title Changed From CN0114 to AN-1578.... Universal  
Changes to Figure 1 ..... 1  
Changes to Circuit Description Section ..... 3

**3/2010—Rev. 0 to Rev. A**

Changes to Circuit Function and Benefits Section ..... 1

**8/2009—Revision 0: Initial Version**

**CIRCUIT DESCRIPTION**

This circuit employs the AD5292 digital potentiometer in conjunction with the AD8221 in-amp, providing an overall low cost, high voltage, programmable gain in-amp.

The differential input signal, +IN and -IN, is amplified by the AD8221. The in-amp offers accuracy, low noise, high CMRR, and high slew rate.

The maximum circuit gain (G) is defined in Equation 1, where R<sub>AW\_MIN</sub> is the wiper resistance of the AD5292 in the rheostat mode and represents the minimum value of the gain setting resistance (100 Ω).

$$G = 1 + \frac{49.4 \text{ k}\Omega}{R_{AB}} \leq 1 + \frac{49.4 \text{ k}\Omega}{R_{AW\_MIN}} \leq 500 \tag{1}$$

where R<sub>AB</sub> is the total resistance across the A and B terminals of the AD5292 in rheostat mode.

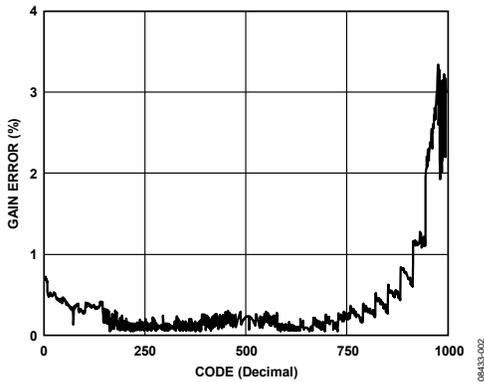


Figure 2. Gain Error vs. Code

The circuit gain formula for any particular AD5292 resistance can be calculated with the following equation:

$$G = 1 + \frac{49.4 \text{ k}\Omega}{(1024 - D) \times R_{AB} / 1024} \tag{2}$$

where D is the decimal code.

Equation 2 is plotted in Figure 3 as a function of the decimal code.

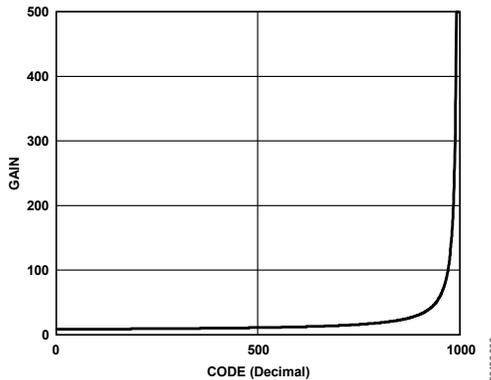


Figure 3. Gain vs. Decimal Code

The maximum current allowed through the AD5292 is ±3 mA, which limits the allowable circuit gain as a function of differential input voltage.

Equation 3 shows the maximum gain limit as a function of the differential input voltage (V<sub>IN</sub>). This equation is derived by substituting R<sub>AB</sub> = V<sub>IN</sub>/3 mA into Equation 1. The result of Equation 3 is plotted in Figure 4.

$$G \leq 1 + \frac{148}{V_{IN}} \tag{3}$$

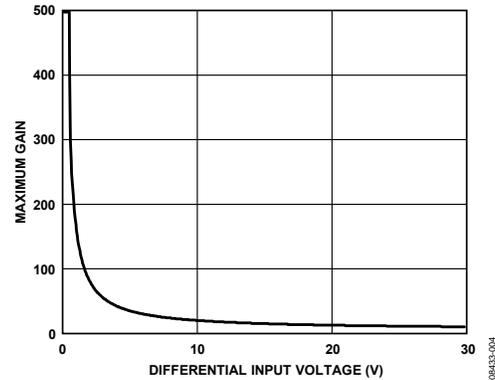


Figure 4. Allowable Gain vs. Differential Input Voltage

Equation 1 limits the maximum circuit gain to 500. Equation 2 can be solved for D, yielding Equation 4, which calculates the minimum allowable resistance (in terms of the digital code) in the AD5292 without exceeding the current limit.

$$D \geq 1024 - \left( \frac{49.4 \text{ k}\Omega \times 1024}{R_{AB} \times (G - 1)} \right) \tag{4}$$

where:

D is the code loaded in the digital potentiometer.

G is the maximum gain calculated from Equation 3.

When the input to the circuit is an ac signal, the parasitic capacitances in the digital potentiometer can cause a reduction in the maximum AD8221 bandwidth. A gain and phase plot is shown in Figure 5.

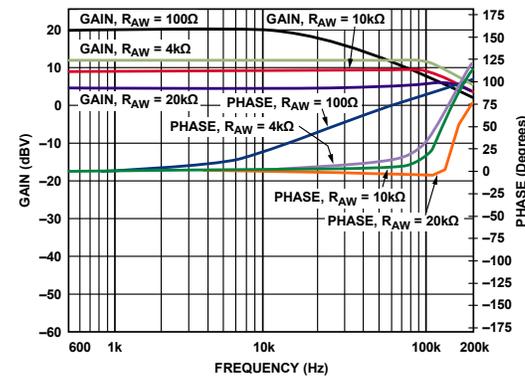


Figure 5. Gain and Phase vs. Frequency (Vertical Scale Compressed to Show All Gain Curves)

The [AD5292](#) has a 20× programmable memory, which allows presetting the output voltage in a specific value at power-up.

Excellent layout, grounding, and decoupling techniques must be used to achieve the desired performance from the circuits discussed in this application note (see [MT-031 Tutorial](#) and [MT-101 Tutorial](#)). As a minimum, use a 4-layer printed circuit board (PCB) with one ground plane layer, one power plane layer, and two signal layers.

### COMMON VARIATIONS

The [AD5291](#) (8 bits with 20× programmable power-up memory) and the [AD5293](#) (10 bits, no power-up memory) are both  $\pm 1\%$  tolerance digital potentiometers that are suitable for this application.

### REFERENCE

- [MT-031 Tutorial. \*Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"\*. Analog Devices.](#)
- [MT-032 Tutorial. \*Ideal Voltage Feedback \(VFB\) Op Amp\*. Analog Devices.](#)
- [MT-061 Tutorial \*Instrumentation Amplifier \(In-Amp\) Basics\*. Analog Devices.](#)
- [MT-087 Tutorial. \*Voltage References\*. Analog Devices.](#)
- [MT-091 Tutorial. \*Digital Potentiometers\*. Analog Devices.](#)
- [MT-095 Tutorial. \*EMI, RFI, and Shielding Concepts\*. Analog Devices.](#)
- [MT-101 Tutorial. \*Decoupling Techniques\*. Analog Devices.](#)