

Maxim > Design Support > Technical Documents > Application Notes > Amplifier and Comparator Circuits > APP 4572 Maxim > Design Support > Technical Documents > Application Notes > Battery Management > APP 4572 Maxim > Design Support > Technical Documents > Application Notes > Circuit Protection > APP 4572

Keywords: reverse battery protection, lithium-ion battery charger, comparators, n-channel FETs

APPLICATION NOTE 4572 Reverse Battery Charger Protection

By: Zeeshawn Shameem, Member of the Technical Staff, Applications Feb 16, 2011

Abstract: Combining a linear-mode single-cell lithium-ion battery charger (MAX1551) with a comparator (MAX9001) and n-channel FET adds a layer of reverse-battery protection that protects a single cell lithium-ion battery charger and battery from damage due to backwards insertion.

A similar version of this article appeared in the March 1, 2007 issue of PET magazine.

Many battery powered applications use diodes for reverse battery protection. However a diode does not always protect a battery charger when the battery is inserted incorrectly. Sometimes when the battery is inserted backwards it can cause a large amount of current flow through the charging circuitry, possibly destroying both the battery and charger. Many battery-charger designs rely on mechanical means that only allow a battery or power plug to be inserted one way. Cell phone batteries are mechanically shaped so that they can be inserted with the proper orientation. Even the charger cord is mechanically shaped to allow insertion in one way.

The simple circuit in **Figure 1** adds another layer of reverse battery protection and protects a single cell lithium-ion battery charger and battery from damage due to backwards insertion. In the circuit, the MAX1551 linear mode single-cell lithium-ion battery charger delivers the charging current to the cell from either an AC adaptor or USB power supply. During normal operation the MAX9001 output is high and the FET is on. When the battery is inserted backwards, the MAX9001 output goes low and the FET turns off, thus blocking current flow. The rapid switching of the FET keeps the current surge to less than 50mA and that surge lasts for less than 200ns before dampening as shown in the lower scope trace (**Figure 2**).



Figure 1. Schematic for simple reverse battery charger protector.



Figure 2. The top curve simulates the insertion of the battery and the bottom curve is the current measured through a Tektronix® current probe.

When the cell is inserted backwards, the potential at the inverting terminal of the MAX9001 increases beyond the supply voltage. Resistor R1 limits the amount of overvoltage current sourced through the onchip electrostatic discharge (ESD) diode. Larger resistor values can be selected to limit the reverse battery leakage current through the ESD diodes, but the tradeoff is slower operation and larger transients. In the test circuit used, $V_{CC} = +5V$ and R1 = R2 = 50k Ω . The low-side FET enables this type of circuit to work for multi-cell batteries as long as the comparator inputs are within the absolute ratings of the comparator. Connecting battery in reverse without the external protection will destroy the MAX1551 due to the high current surge.

Tektronix is a registered trademark and registered service mark of Tektronix, Inc.

Related Parts		
MAX1551	SOT23, Dual-Input, USB/AC Adapter, 1-Cell Li+ Battery Chargers	Free Samples
MAX9001	Low-Power, High-Speed, Single-Supply Op Amp Comparator Reference ICs	Free Samples

More Information

For Technical Support: http://www.maximintegrated.com/support For Samples: http://www.maximintegrated.com/samples Other Questions and Comments: http://www.maximintegrated.com/contact

Application Note 4572: http://www.maximintegrated.com/an4572 APPLICATION NOTE 4572, AN4572, AN 4572, APP4572, Appnote4572, Appnote 4572 Copyright © by Maxim Integrated Products Additional Legal Notices: http://www.maximintegrated.com/legal